

**Answer the following questions****10 Marks****Question 1**

- (a) We need to introduce (Al) atoms as impurities for a shallow depth in the Si semiconductor. Explain -with draw- the suitable method for that?
- (b) What is meant by (annealing)?
- (c) A silicon wafer has an Bi doping density of  $10^{22} \text{ m}^{-3}$  at 300 °K. What is the resistivity of the wafer?  $\mu_n = 0.135 \text{ m}^2/\text{V.sec}$

**Question 2****10 Marks**

- (a) Explain -with draw- the most common method used to determine type of conductivity of the S.C. material. When this method is not applicable?
- (b) Why the Haynes Shockley Experiment was limited in the first days to the germanium atoms only?
- (c) A noninjecting metal probe of 1 mm diameters is placed on a plane surface of a semiconductor of  $25 \Omega\text{-cm}$  resistivity. The outer surface of the semiconductor has an ohmic contact. a 2 V battery is connected between the probe and the ohmic contact. Neglecting the voltage drop across the metal and the ohmic contact, determine the current flowing through the circuit.

WITH BEST WISHES  
DR. MOHAMED SALAH

Part1

Answer the following questions

Q1( 15 Marks)

- 1-a- What is meant by class A amplifier? .  
Show that its maximum efficiency is 25%.

1-b- Find the maximum ac output power, the dc input power and the maximum efficiency of the amplifier shown in Fig. 1. Also determine the input resistance assuming  $\beta_{ac}=50$  and  $r'_e=6\Omega$ .

If the circuit shown in Fig. 1 is replaced by a Darlington class AB push-pull amplifier with  $\beta_{ac}=50$  for each transistor, what will be the input resistance?, and , what is the advantage of that? .

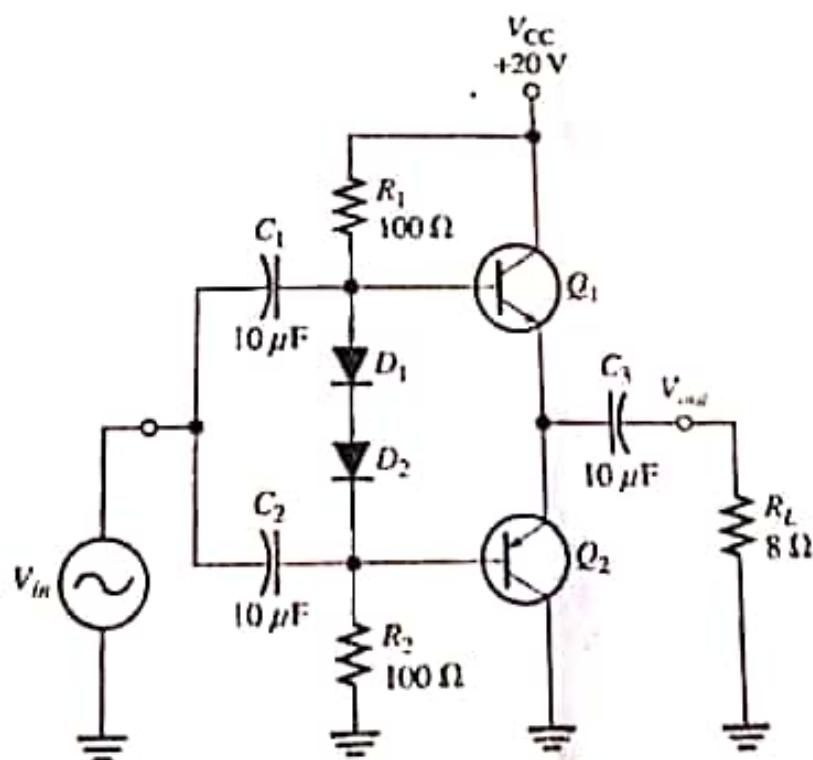


Fig. 1

**Answer the following questions****10 Marks****Question 1**

- (a) We need to introduce (N) atoms as impurities for a shallow depth in the Si semiconductor. Explain -with draw- the suitable method for that?
- (b) What is meant by (annealing)?
- (c) A silicon wafer has an Bi doping density of  $10^{22} \text{ m}^{-3}$  at 300 °K. What is the resistivity of the wafer?  $\mu_s = 0.135 \text{ m}^2/\text{V sec}$

**Question 2****10 Marks**

- (a) Explain -with draw- the most common method used to determine type of conductivity of the S.C. material. When this method is not applicable?
- (b) Why the Hoynes Shockley Experiment was limited in the first days to the germanium atoms only?
- (c) A noninjecting metal probe of 1 mm diameters is placed on a plane surface of a semiconductor of  $25 \Omega\text{-cm}$  resistivity. The outer surface of the semiconductor has an ohmic contact. a 2 V battery is connected between the probe and the ohmic contact. Neglecting the voltage drop across the metal and the ohmic contact, determine the current flowing through the circuit.

**WITH BEST WISHES**  
DR. MOHAMED SALAH

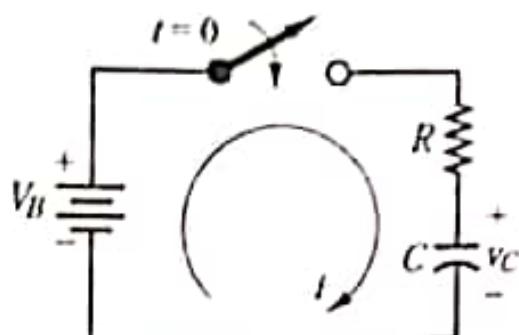


Figure 1

**Question – 3:** For the ac power circuit shown in Figure 2,

- Determine the power triangle.
- Determine the current supplied by the source.


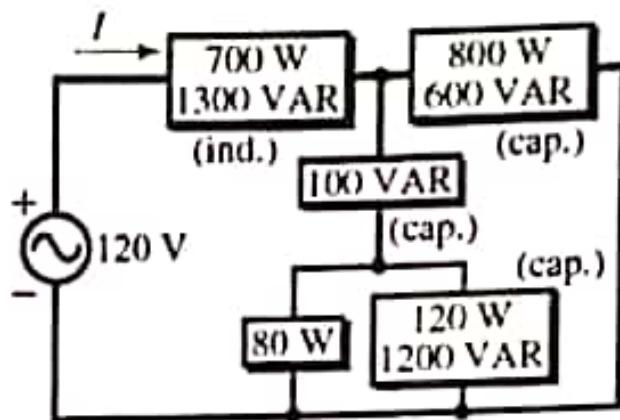


Figure 2

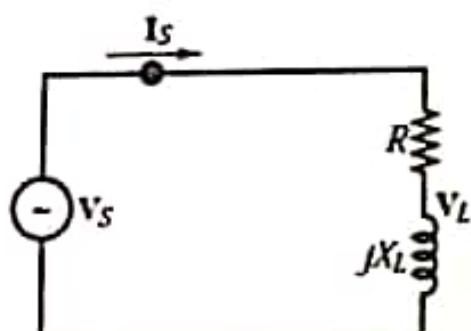**Question – 4:** For the circuit shown in Figure 3, if  $V_s = 117\angle0^\circ \text{ V}$ ,  $R_L = 50 \Omega$ ,  $X_L = 86.7 \Omega$  and  $f = 60 \text{ Hz}$ . Calculate the complex power and correct the power factor to unity.



Minoufia University  
Faculty of Electronic Engineering  
Dept. Industrial Electronics and Control Eng.  
Course: Electrical Power  
Course Field: Specialization Requirements  
Academic Level: First Year, 2<sup>nd</sup> Semester  
Academic Year: 2017 / 2018  
Course Code: ACE 124



Midterm Exam  
Date: 24 / 3 / 2018  
Exam Type: Written  
No. of Exam Pages: 2  
No. of Exam Questions: 3  
Exam Marks: 20 Marks  
Exam Time: 60 Minutes  
From 12:30 AM to 1:30 AM

Name:

Class:

*Answer the following questions:*

Question - 1: Put True (✓) or False (✗) signs for the following expressions:

1.	Nuclear power stations of generating electricity have cheaper initial cost, but expensive running cost.	(   )
2.	The non-conventional energy sources are further advantageous due to virtually zero running cost.	(   )
3.	A fuel cell has an ac output voltage typically of 1.23 volts at normal atmospheric pressure and temperature.	(   )
4.	A nuclear power plant is a thermal power station in nature.	(   )
5.	Wind power stations is a non-conventional sources of electrical power that have exclusive advantages of being pollution free and renewable.	(   )
6.	Raising the voltage makes it possible to transmit large amounts of electric power over long distances with minimum line losses.	(   )
7.	Hydroelectric power stations are considered non-conventional sources of electrical power generation.	(   )
8.	The nuclear generation of electric power is disadvantageous due to high capital cost as well as the maintenance charges.	(   )
9.	Fuel cells operate based on the photo-voltaic effect, which develops an emf. on absorption of ionizing radiation from Sun.	(   )
10.	When selecting a method of generating electricity, it is naturally desirable that the source must have not perpetuity.	(   )

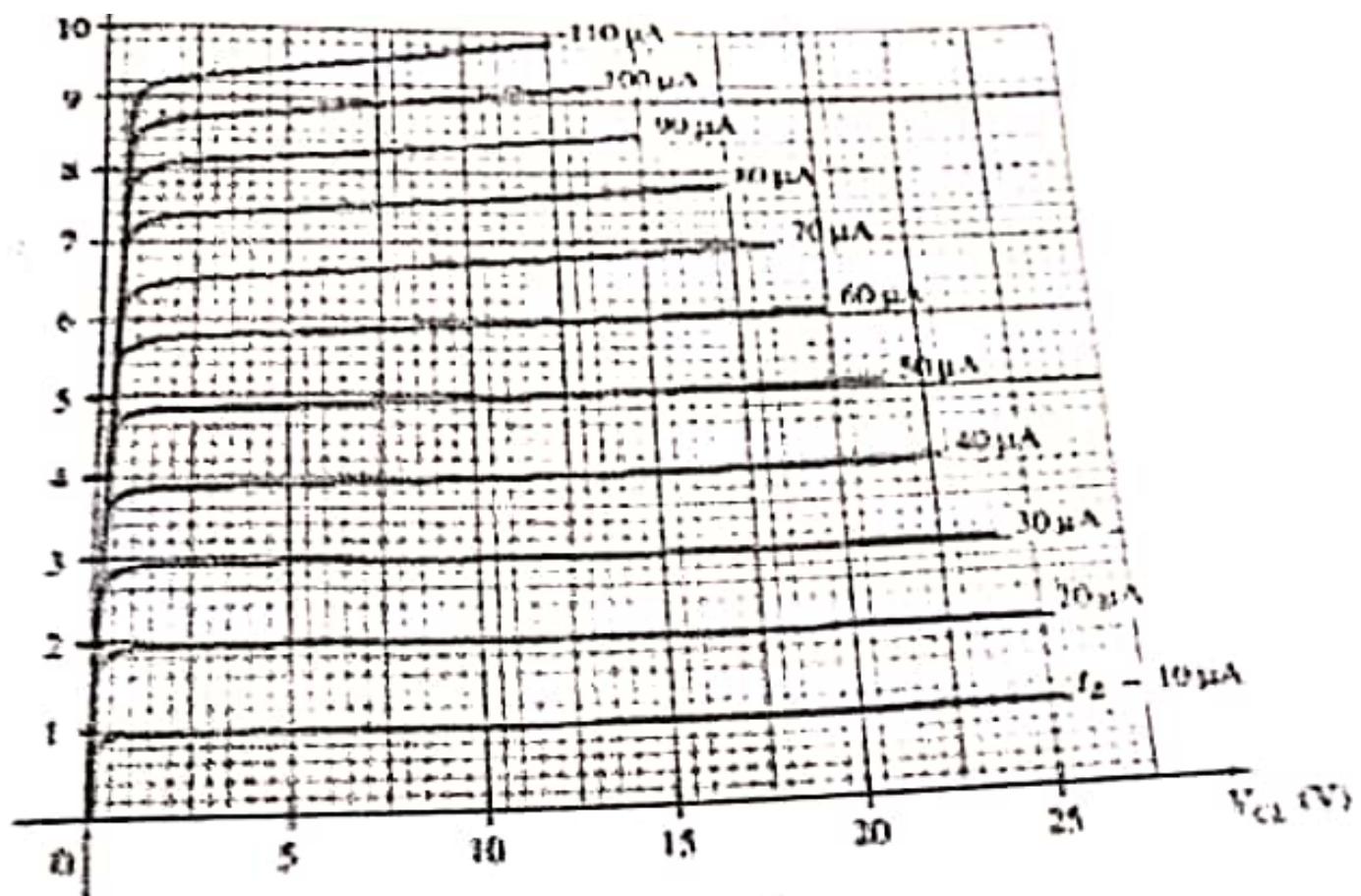


Fig. (1-3)

- 2) For the circuit shown in Fig.2.

(10 marks)

$$V = V_0 \sin \omega t$$

- Find an expression for the circuit impedance.
- Drive an expression for instantaneous power ( $P_i$ ) and average power ( $P_{avg}$ ) delivered by the source.
- Find the value of  $\omega$  that makes the impedance minimum.

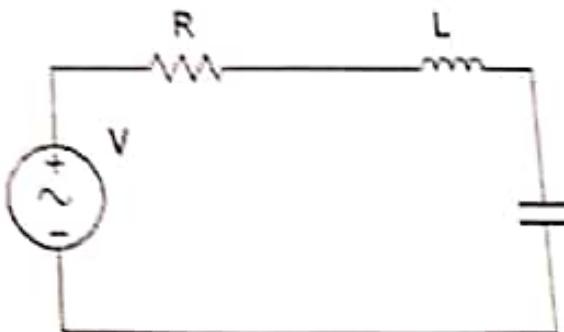


Fig.2

- Q2(a)** For the circuit shown in fig (3) draw the output waveform if
- Both S1 and S2 open.
  - S1 open and S2 closed.
  - S1 closed, and S2 open.
  - Both S1 and S2 closed.
- (b) If  $R_L = 1k\Omega$  and  $C = 100\mu F$  with both S1 and S2 closed calculate.
- The ripple voltage and the ripple factor.
  - The dc output voltage.

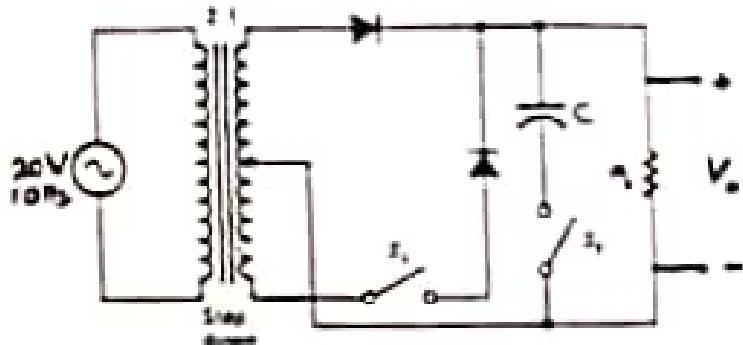


Fig.(3)

دقيق من

المرنة العزل

ذكاء وروبوتات (١)


كتاب (أونلاين) بـ ذكاء وروبوتات  
قسم ذكاء وروبوتات  
جامعة بور سعيد - مصر

تم إطالق

الصلح


Answer the following questions:

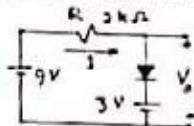Q1-(a) Calculate I & V<sub>o</sub> for each circuit of Fig(1). Consider ideal diodes.



(a)

Fig(1)

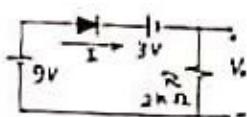


(b)

Q1-(b) For the logic circuit shown in Fig(2):

-What is the function of the circuit.

-Draw the output waveform.

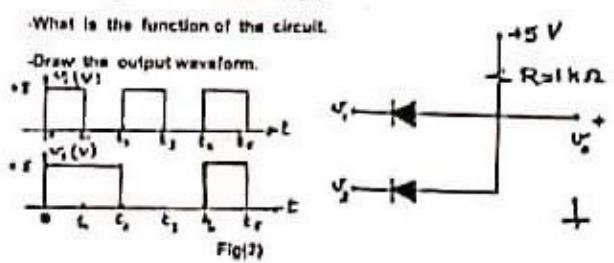

Fig(2)



**Q1:** For the circuit of figure (1). A number of Nickel-Cadmium voltage cells of an internal resistance ( $r_i = 0.2 \Omega$ ) and capacity of ( $C_i = 10 Ah$ ) per cell, has been connected to form a single battery  $E_B$  of e.m.f ( $E_B = 24V$ ) and ( $C_B = 20 Ah$ ). Answer the following points:

(7 Marks)

- 1) What is the total number of voltage cells used?
- 2) Draw the connection diagram of the voltage cells.
- 3) If the battery  $E_B$  is used to drive the motor of an electric car a distance of 2km with a constant speed of 100m/h for an average motor current of 0.5A. What is the capacity of  $E_B$  after travelling this distance?
- 4) Determine the current  $I_1$  flowing in the circuit of figure (1) after closing sw. ( $R_2 = 8 \Omega$ )
- 5) Determine the value of  $V_a$ ,  $V_b$  and  $V_c$  before and after closing sw.


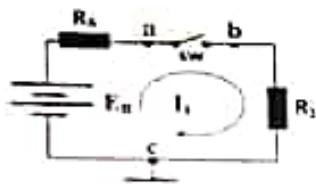


Fig. (1)

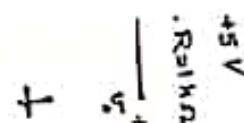
[ Note that: the e.m.f of the Ni-Cd voltage cell  $E_i = 1.2 V$  ].



(8 Marks)

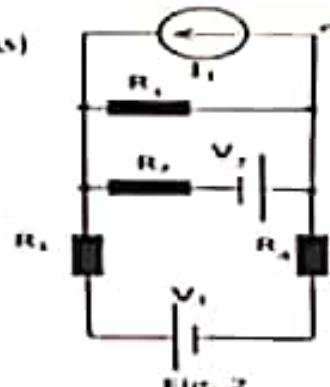
**Q2:** For the circuit of figure (2). Using the nodal analysis, determine the power dissipation in the resistance  $R_2$ .

[ where:  $R_1 = 50 \Omega$ ,  $R_2 = 100 \Omega$ ,  $R_3 = 0.2 \text{ k}\Omega$ ,  $R_4 = 0.25 \times 10^{-3} \text{ M}\Omega$ ,  $V_1 = 10V$ ,  $V_2 = 20V$ ,  $I_t = 2A$  ].



(5 Marks)

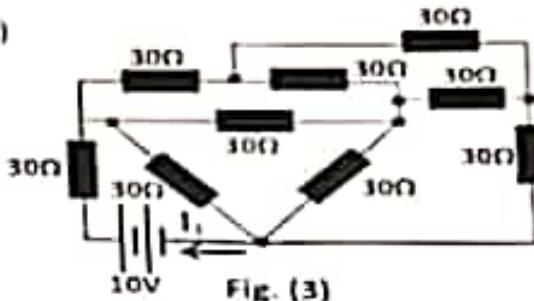Q1: For the circuit of figure (3). Determine the value of the current  $I_1$  using resistance aggregation and Ohm's law.





Q1: For the circuit of figure (1). A number of Nickel-Cadmium voltage cells of an internal resistance ( $r_i = 0.2 \Omega$ ) and capacity of ( $C_i = 10 Ah$ ) per cell, has been connected to form a single battery  $E_B$  of e.m.f ( $E_B = 24V$ ) and ( $C_B = 20 Ah$ ). Answer the following points: (7 Marks)

- 1) What is the total number of voltage cells used?
- 2) Draw the connection diagram of the voltage cells.
- 3) If the battery  $E_B$  is used to drive the motor of an electric car a distance of  $2km$  with a constant speed of  $100m/h$  for an average motor current of  $0.5A$ . What is the capacity of  $E_B$  after travelling this distance?
- 4) Determine the current  $I_f$  flowing in the circuit of figure (1) after closing sw. ( $R_f = 8 \Omega$ )
- 5) Determine the value of  $V_{ac}$ ,  $V_{ab}$  and  $V_{bc}$  before and after closing sw.

[ Note that: the e.m.f of the Ni-Cd voltage cell  $E_c = 1.2 V$  ].

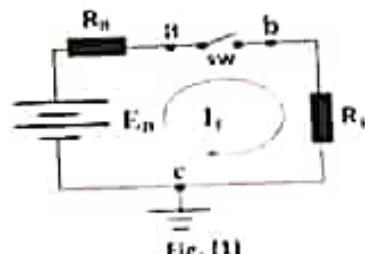


Fig. (1)

*Third question: (5 marks)*

- a) By using dynamic memory, write a program to find the minimum and the maximum values in a dynamic array of N integer numbers. Print on the screen the minimum and the maximum values. (5 marks)

*Best wishes \**

```
while (current != NULL)
{
    temp = current->next;
    current->next = prev;

    prev = current;
    current = temp;
}

head = prev;
```

Assume that reference head of a linked list contains A  $\leftrightarrow$  B  $\leftrightarrow$  C  $\leftrightarrow$  D  $\leftrightarrow$  E  $\leftrightarrow$  F is passed to above function. What should be the modified linked list after the function call?

- (b) By assuming a linked list of N nodes containing integer data, write a function to insert a node in the linked list after the node that has data equals 50. (5 marks)

```

//using <iostream>
using namespace std;
int main()
{
    int num[5];
    int* p;
    p = num;
    *p = 10;
    p++;
    *p = 20;
    p = &num[2];
    *p = 30;
    p = num + 3;
    *p = 40;
    p = num;
    *(p + 4) = 50;
    for (int i = 0; i < 5; i++)
        cout << num[i] << ", ";
    return 0;
}

```

## *Second question: (9 marks)*


- (a) Consider the following function that takes reference to head of a Linked List as parameter. Assume that a node of linked list has a pointer to next node as *next*. (4 marks)

```

struct Node
{
    char C;
    Node* next;
};

void function(Node *head)
{
    Node *current = head;
    Node *temp = NULL;
    Node *prev = NULL;
}

```

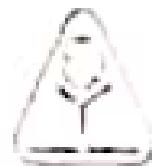

NAME:

Section:

*Answer the following questions:*

*First question: (6 marks)*

- a) Rewrite the following program after removing the errors. Underline each correction.: (6 marks)

Program	Correction
#include <iostream> using namespace std; struct Pixel { int color, style; }; void showPoint(Pixel P) { cout << P.color, P.style << endl; } int main() { Pixel Point1 = {5, 3}; showPoint(Point1); Pixel Point2 = Point1; color.Point1 += 2; showPoint(Point2); return 0; }	

Menofia University  
Engineering Physics Department  
First Year- First Term  
Date 29-10-2018  
Full Mark: 30

Faculty of Electronic Engineering  
Engineering Physics 3  
Mid Term Exam  
Time: 1hr

Physical Constants:  
 $m_e = 9.1 \times 10^{-31} \text{ Kg}$      $e = 1.6 \times 10^{-19} \text{ C}$      $\hbar = 6.6 \times 10^{-34} \text{ Js}$      $c = 3 \times 10^8 \text{ m/s}$   
 $k = 1.38 \times 10^{-23} \text{ J/K}$

Answer the Following Questions:

- 1) Consider an electron of mass ( $m$ ) moving in  $xy$ -plane in a two-dimensional box of side lengths ( $L$ ), such that ( $V=0$ ) inside and ( $V=\infty$ ) outside the box.

Find the eigen-functions and the eigen-values.

[ 12 Marks ]

- 2) Discuss the mathematical and physical meaning of the four quantum numbers.

[ 8 Marks ]


3. ) Electrons with a maximum kinetic energy of 3eV are ejected from a metal surface by ultraviolet radiation of wavelength 1500A. Find:


- i) The work function of the metal
- ii) The threshold wavelength of the metal
- iii) The stopping potential

[ 10 Marks ]

Good luck

Dr.Ahmed Abo Arais

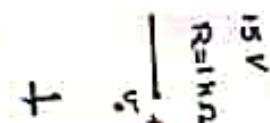

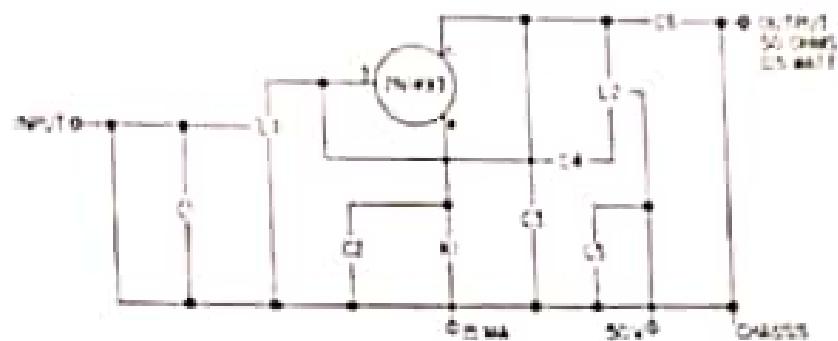

The transistor is of the NPN type.  $C_1$ ,  $C_2$ ,  $C_3$ , and  $L_1$  are variable.  
 $L_1$  and  $L_2$  have fixed taps.



الجواب

سلسلة رقم (٢) مع التفاصيل بالتفصيل و التفاصيل .


أجب عن الأسئلة الآتية : (Free Hand)


دrew all the : ( ١٠ درجات )

اكتب اسماء الرموز التالية:

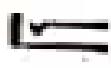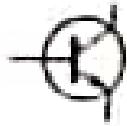

رسم رموز المكونات التالية:

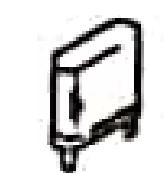

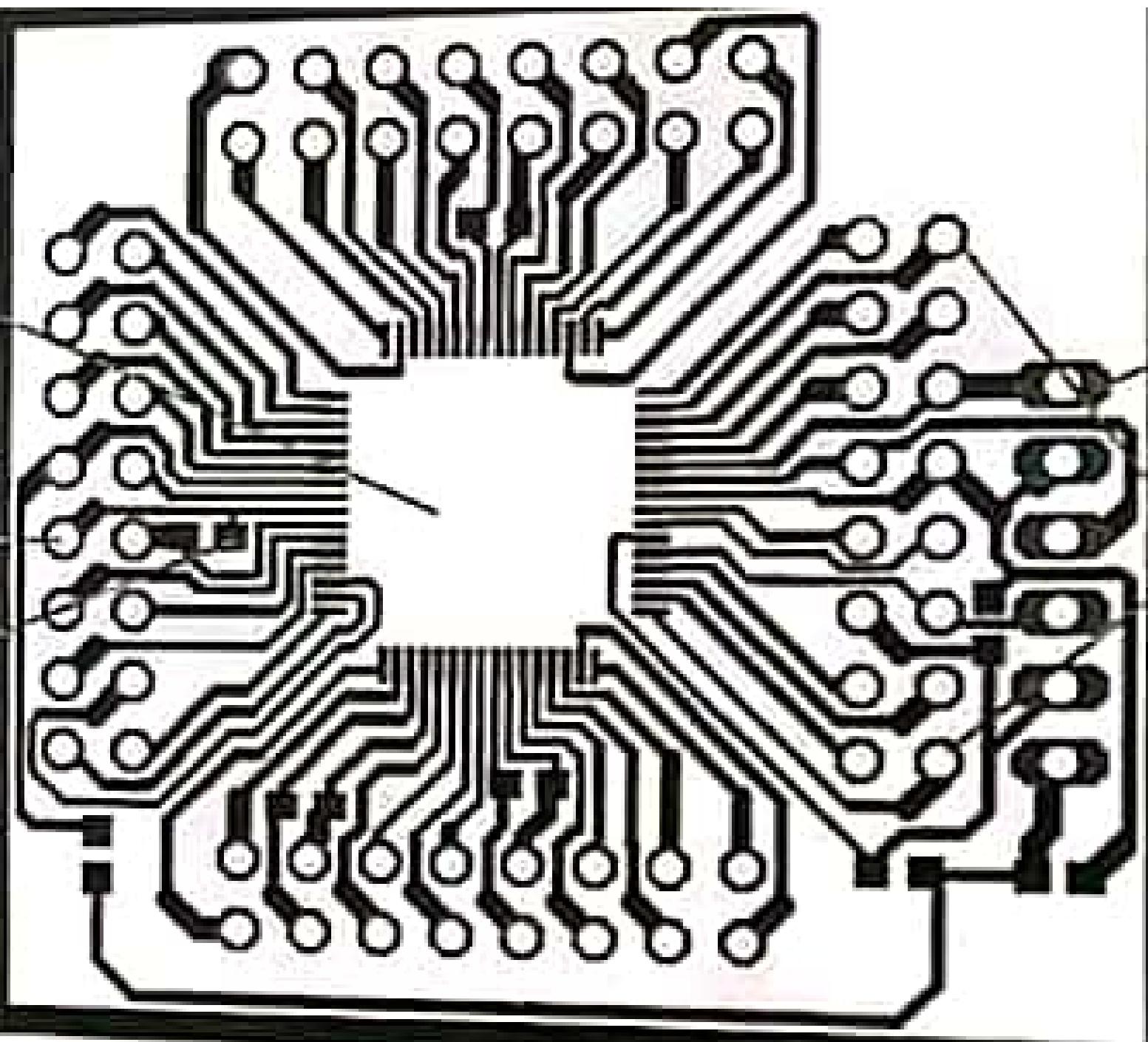

عنصر الالكتروني الذي سببت له العطلة ١ هو ( عنصر متعدد - عنصر مطعّم )  
عنصر الالكتروني المتعرض في عطلة رقم ١ بـ ( ..... ) طرف  
العنصر الالكتروني المتعرض في عطلة رقم ٢ بـ ( ..... ) طرف

**العنصر الانتحيри لعناصر التثبيت السطحي SMD بمن الألتحيري**

<b>Surface Maintain Devices</b>	<b>Surface Mount Devices</b>
---------------------------------	------------------------------

<b>Surface Made Devices</b>	<b>Surface Mount Designs</b>
-----------------------------	------------------------------

نوع الدائرة المطبوعة الخام PCB هو مساراً عن لوح تدوير تعلق متصل عليه

<b>بـ- الطبقات التحليمية بعد تشكيفها</b>	<b>أـ- الطبقات التحليمية قبل تشكيفها</b>
--	--

<b>دـ- لا يوجد إجابة صحيحة</b>	<b>جـ- الطبقات التحليمية مع تشكيفها</b>
--------------------------------	---

**النموذج الأولي Prototype** لأن دائرتين أو حفلاً هو

<b>بـ- النماذج الأولى نوع الترتيب التتابع</b>	<b>أـ- نوادرات تصميم أو خط التتابع</b>
---	--

<b>دـ- مثل ما سبق</b>	<b>جـ- دراسة خطوات التصنيع الأولى تحيل</b>
-----------------------	--

شكل بخطه تمام طرف العنصر ليس لها الهرولة (LBBM) يستخدم لربط المعاينات والتحكم بهما

<b>بـ- لعناصر التثبيت</b>	<b>أـ- لعناصر التثبيتية</b>
---------------------------	-----------------------------

<b>دـ- لا يوجد إجابة صحيحة</b>	<b>جـ- توسيع نقطة الأرض بمتداورة المطبوعة</b>
--------------------------------	---

**بشر واجها التحكم Control Panel** البرنامج المستخدم في تصميم لوح المطبوع

<b>بـ- مدخل البرنامج</b>	<b>أـ- مرتكز تحكم البرنامج</b>
--------------------------	--------------------------------

<b>دـ- لا يوجد إجابة صحيحة</b>	<b>جـ- كلبة البرنامج</b>
--------------------------------	--------------------------

---

Answer all of the following questions

Question (1):

(10 Marks)

a) Find the Laplace transform of the following functions.

$$1). f(t) = \sinh^2(3t) + 3t^3 - 5t$$

$$2). f(t) = t^3 e^{4t} + 3t^2$$

$$3). f(t) = t e^{-3t} \cos(\omega t)$$

$$4). f(t) = \begin{cases} 1, & 0 < t < 1 \\ -1, & 1 < t < 2 \end{cases}; \quad T = 2$$

b) Write the function  $f(t)$  in terms of unit step function, then find its Laplace transform.

where  $f(t) = \begin{cases} 2, & 0 \leq t < 1 \\ t, & 1 \leq t \leq 5 \end{cases}$

Question (2):

(10 Marks)

Find the inverse Laplace transform for the following functions:

$$1). F(s) = \frac{2s+4}{s^2 + 1}$$

$$2). F(s) = \frac{3s-4}{(s+2)^3(s-1)}$$

$$3). X(s) = \frac{s^2+1}{s^2+s-2} e^{-3s}$$

$$4). F(s) = \frac{(1-e^{-s})}{s(1+e^{-s})}$$

<i>جامعة المنيا</i>	<i>كلية الهندسة</i>
<i>University</i>	<i>Menoufia</i>
<i>Faculty</i>	<i>Electronic Engineering</i>
<i>Department</i>	
<i>Academic level</i>	<i>1<sup>st</sup> Year</i>
<i>Course Name</i>	<i>Electronics I</i>
<i>Course Code</i>	
<i>Date</i>	<i>24/1/2019</i>
<i>Time</i>	<i>3 Hours</i>
<i>No. of pages</i>	
<i>Full Mark</i>	<i>60 Marks</i>
<i>Exam</i>	<i>Final Exam</i>
<i>Examiner</i>	<i>Prof. Dr. El-Dokany Dr. M Zien</i>

*part (I) 30 Marks Prof. Dr. El-Dokany*

*Answer all the following questions (30 degrees)*

**Question No 1:** How we can express such expressions, (10 degrees)

(a) Forward voltage, Reverse voltage, Cut-in Voltage, cut off voltage, Peak-inverse Voltage (5 degrees)

(b) Consider a silicon crystal whose band gap energy is  $E_g = 1.12 \text{ eV}$  and its temperature are kept at  $T = 300 \text{ K}$ .

1. If the Fermi level,  $E_F$ , is in the middle of the band gap, what is the probability to found electron at  $E = E_c + kT$ . (2.5 degrees)

2. If the Fermi level,  $E_F$  is located at the conduction band edge,  $E_F = E_c$ , what the probability to find an electron at  $E = E_c + kT$ . (2.5 degrees)

**Question No 2:** (10 degrees)

(a) We know that, for electronic uses, the most important property of semiconductor material is that its conductivity be modulate by external signals, can you determine which parameter that effect the conductivity? (5 degrees)

(b) What are the main factors affecting the mobility of charge carriers in semiconductors? (5 degrees)

**Question No 3:** (10 degrees)

A. (a) How PN junction comes in equilibrium statement? (4 degrees)

(b) Consider Silicon abrupt p-n diode with  $N_s = 10^{18} \text{ cm}^{-3}$  and  $N_d = 10^{16} \text{ cm}^{-3}$ . Calculate the junction capacitance at 3V, diode area equals  $10^{-4} \text{ cm}^2$ , Si intrinsic concentration is  $10^{10}$ , Si relative permeability is 16, free space permittivity is  $8.87 \times 10^{-15} \text{ F/cm}$ , electronic charge is  $1.6 \times 10^{-19}$ ,  $KT/q = 1/40$ , The constant for material properties (a) equal two

B. Calculate the built-in potential of the diode? Calculate the depletion layer thickness in each side of the junction?, the total depletion layer thickness?, the depletion region capacitance in both cases (alloyed junction and diffused junction)? (6 degrees)

*With my best wishes*

Page 1 of 1

- الجواب**
- 4.a) Briefly discuss nanostructures in terms of their dimensionality. [5Marks]
- 4.b) What are the confinement regimes for quantum dots with infinite potential barriers? [5Marks]
- 4.c) What are the possible applications of nanostructures? [5Marks]
- .....

5.a) How are X-rays generated? Describe the construction and operation of Coolidge X-ray tube. How are intensity and hardness of X-rays controlled? [5Marks]

5.b) Why exposure to X-ray injurious to health but exposure to visible light is not, when both are electromagnetic waves? [5Marks]

5.c) What is the coordination number? Calculate the coordination number for simple cubic, bcc and FCC lattices? [5Marks]

.....

6.a) Explain why the properties of polycrystalline materials are most often isotropic? [5Marks]

6.b) Briefly discuss the similarities and difference between photons and phonons. [5Marks]

6.c) Briefly explain why some transparent materials appear colored whereas others are colorless. [5Marks]

.....

مع خالص امنيات بالتفوق والنجاح ا.د. سناه محمود الريبيسي.

- 
- 1-a) Explain the physical meaning and the properties of the wave function ( $\psi$ ) according to quantum theory. [5Marks]
- 1-b) Consider an electron of mass (m) moving in x-direction in an infinite potential well of width (L), such that ( $V=0$ ) inside and ( $V=\infty$ ) outside the well. Find and draw the eigenfunctions, the eigenvalues and the probability of finding the electron for  $n = 1, 2, 3$ . [5Marks]
- 1-c) Calculate the amount of energy emitted radiation when an electron in a three-dimensional box of side length 0.5nm makes transition from the third excited state to the first excited state. Find the corresponding wavelength of the emitted radiation. [5Marks]

- 
- 2-a) Define: 1-Degeneracy    2-Zeeman effect    3-Fermi energy level  
4-Pauli exclusion principle 5-Heisenberg uncertainty principle [5Marks]
- 2-b) Plot the energy of electrons (E) against the wave number (k) for free electron theory and band theory. Then show the first and second Brillouin zones. [5Marks]
- 2-c) Calculate the probability of electron occupancy for state whose energy is:  
i) 0.1eV above Fermi energy level. ii) 0.1eV below Fermi energy level.  
iii) equal to Fermi energy level.  
Assume the temperature of 800K. [5Marks]

2. a. Derive The instantaneous power entering a circuit pt)
2. b. The voltage across a load is  $v(t) = 6.0 \cos(\omega t - 10^\circ)$  V and the current through the element in the direction of the voltage drop is  $i(t) = 1.5 \cos(\omega t + 50^\circ)$  A. Find:  
(a) the complex and apparent powers.  
(b) the real and reactive powers, and (c) the power factor and the load impedance.

(10 Marks)

2-1) For the electrical circuit of Fig. 2, determine:

- The equivalent resistance which is seen by the source 100V.
- The voltage drop 'V' across the  $35\ \Omega$  resistance.
- Thevenin equivalent circuit across the  $30\ \Omega$  resistance.

2-2) If the battery of Fig. 3 is connected to the circuit of Fig. 4. Determine the current supplied by the battery when:

- The battery is connected across the terminals a-b.
- The battery is connected across the terminals c-d.

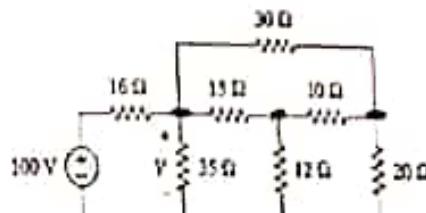


Fig. 2

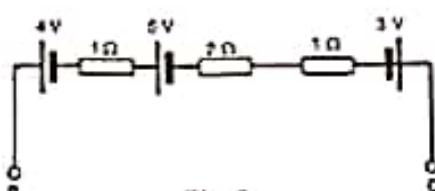


Fig. 3

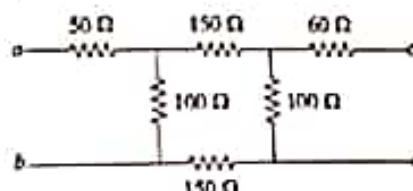


Fig. 4

Q3:

(10 Marks)

3-1) For the electrical circuit of Fig. 5. Determine:

- The value of  $R$  for a maximum power ' $P_{max}$ ' of 3 mW delivered to  $R_L$ .
- The value of  $R_L$  for this condition.
- The value of  $P_{max}$ .

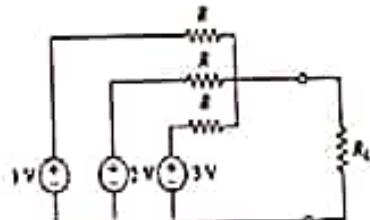


Fig. 5

3-2) For the electrical circuit of Fig. 6, determine the total power delivered to the circuit by the two sources using the super-position principle.

3-3) For the circuit of Fig. 7. Determine the matrix form of the mesh equations.

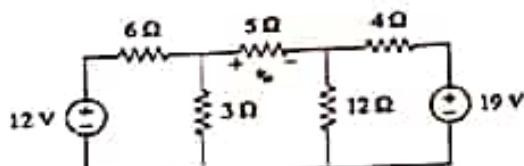


Fig. 6

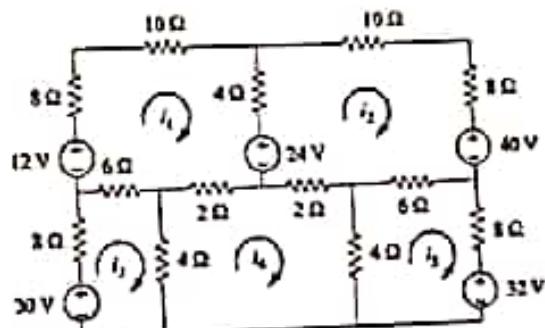


Fig. 7

End of part I

Page (2)





### Part 1: DC Circuit Analysis

**Q1: Choose the most correct answer from the multiple choices (10 Marks)**

1. .... is the type of materials which has a negative temperature coefficient of resistance.  
(a) metals (b) alloys (c) semiconductors (d) insulators (e) None of such choices
2. A wire of aluminum of 100 meters long, 1 mm<sup>2</sup> cross-section, has a conductance of ..... S. ( $\rho_{Al} = 2.8 \times 10^{-8} \Omega \cdot m$ ).  
(a) 2.8 (b) 1.4 (c)  $7 \times 10^{-3}$  (d)  $36 \times 10^{-2}$  (e) None of such choices
3. A coil has a total resistance of 20 Ω at 0 °C, its resistance becomes ..... Ω at 373 °K assuming the material of the coil wire has  $\alpha_0 = 4.26 \times 10^{-3}/^{\circ}\text{C}$ . (note that: T °K = t °C + 273).  
(a) 31.8 (b) 28.5 (c) 212.8 (d) 11.5 (e) None of choices
4. The circuit of Fig. 1 has ..... independent current sources and ..... dependent voltage sources.  
(a) 2 / 1 (b) 1 / 2 (c) 0 / 2 (d) 2 / 0 (e) None of such choices
5. An 100 Vdc source is connected to a group four parallel bulbs of 200V / 100 watt each. The source supplies a current of ..... mA.  
(a) 4000 (b) 1000 (c) 400 (d) 100 (e) None of such choices
6. The polarization in a voltage cell has the effect of ..... its internal resistance.  
(a) fixing (b) increasing (c) decreasing (d) changing (e) None of choices
7. Lead-acid cell is one of the ..... cells.  
(a) primary (b) secondary (c) dry (d) high-resistive (e) None of choices
8. The Li-ion cell has ..... capacity compared to the nickel-cadmium cell.  
(a) equal (b) lower (c) higher (d) linear (e) None of choices
9. Three identical voltage cells are parallel connected to form a battery. Each cell has an open circuit voltage of 5V and internal resistance of 0.6 Ω. The battery terminal voltage for 1A load is equal to ..... V.  
(a) 13.2 (b) 4.8 (c) 14.4 (d) 4.4 (e) None of choices
10. The capacity of the voltage cell is measured by .....  
(a) watt (b) Wh (c) VA (d) Ah (e) None of choices


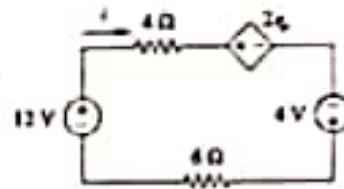


Fig. 1
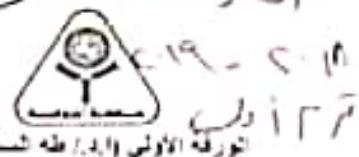
# ال詢

المادة: رسم الدوائر والدوائر الإلكترونية  
 عدد ملحوظات الأسئلة: (1)  
 درجة الورقة الأولى: (30 درجة)  
 زمن الورقة الأولى: ساعة ونصف



كتبة الهندسة الإلكترونية بمعرفة  
 امتحان الفصل الدراسي الأول  
 الفرقه الأولى : 2018/2018  
 تاريخ الامتحان: 3 / 1 / 2019




الورقة الأولى (1) - ٢٠١٩

الورقة الأولى (1) - ٢٠١٩

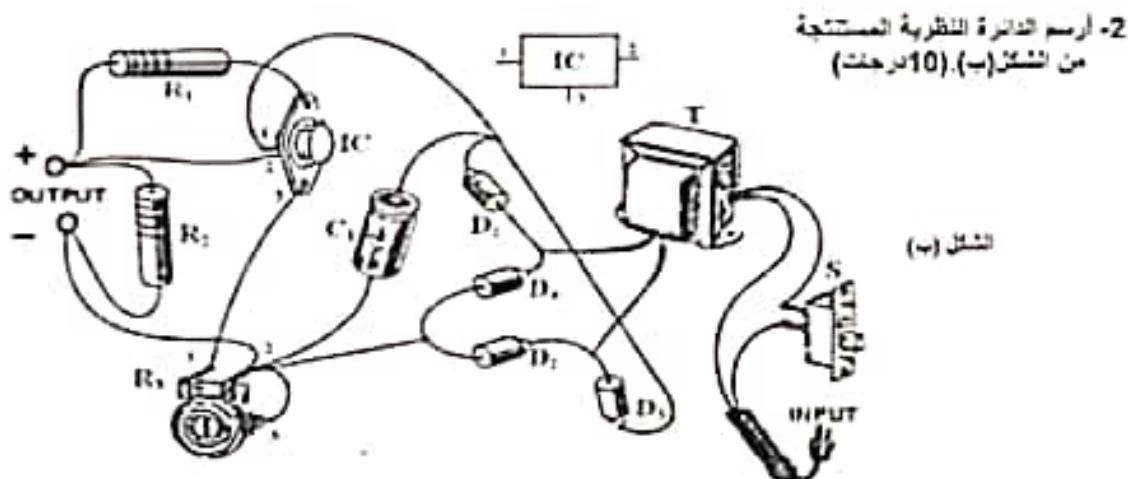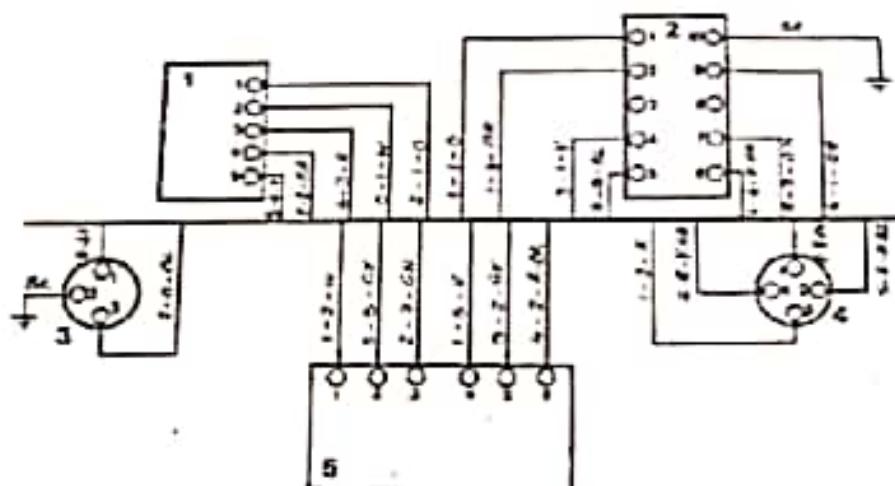ملحوظات هذه: - تقسم الورقة إلى أربعة أقسام ويدعى كل قسم بـ "شلل". - تراعي قواعد رسم الدوائر الإلكترونية مع استخدام الأسلوبات الهندسية



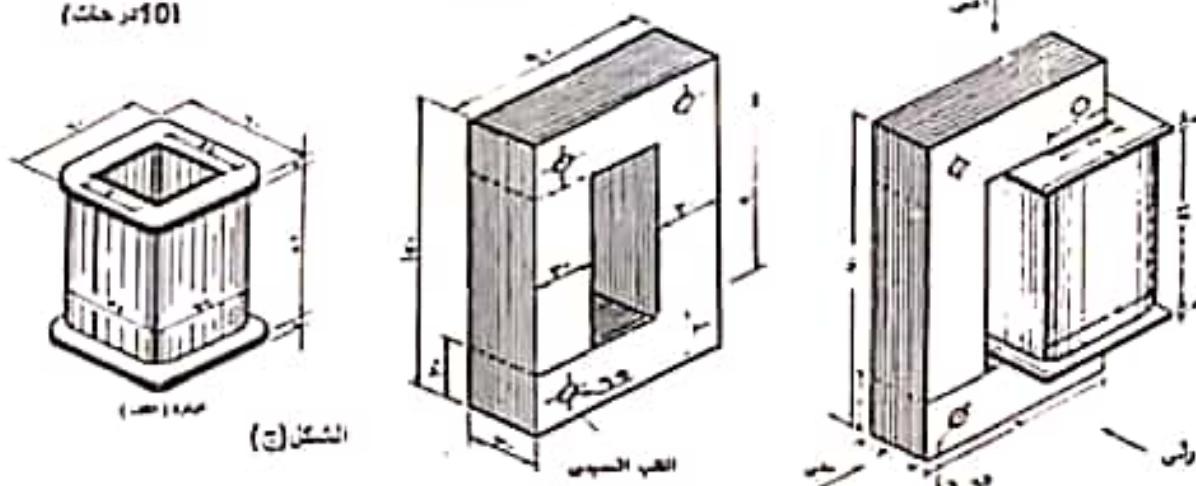**3- الشكل (ج) بين مجمع وأجزاء ملف خلق والمطلوب رسم مخطط راس فضاء كامل عند المتنصف بخطbis رسم مناسب.**  
 (10 درجات)



مع التمنيب بتتوافق والنجاح انتظر الورقة الثانية للدكتور / حسن الأبيض



**PART II Laplace Transforms and Their Applications**

---

**Question (1)**

{20 Marks}

- a) Find Laplace transform of the following functions:

1.  $f(t) = t^n e^{\alpha t}$

2.  $f(t) = \frac{1}{\sqrt{t}} + \sin^2(\pi t)$

3.  $f(t) = \begin{cases} 3e^t, & 0 \leq t \leq 2 \\ 0, & \text{otherwise} \end{cases}$

4.  $f(t) = \int_0^t e^{t-s} \sin(\omega s) ds$

- b) Find the inverse Laplace transform for the following functions:

1.  $F(s) = \frac{1}{\sqrt{s}} + \frac{2}{s^2} + \frac{5s+1}{s^3}$

2.  $F(s) = \frac{s^2 + 1}{s^2 + 2s^2 + s + 2} e^{-s}$

3.  $F(s) = \frac{3s-4}{(s+2)^2(s-1)}$

4.  $F(s) = \frac{(s+1)^2}{(s+2)^3}$

**Question (2)**

{20 Marks}

- a. The  $RLC$  circuit shown in Fig. 1 consists of a resistor  $R = 160 \Omega$ , a capacitor  $C = 10^{-4} F$  and an inductor  $L = 1 H$  connected in series together with a voltage source  $e(t) = 10 V$ . Prior to closing the switch at time  $t = 0$ , both the charge on the capacitor and the resulting current in the circuit are zero. Find:

1. The differential equation governing the charge  $q(t)$  on the capacitor.
2. The current  $i(t)$  in the circuit at any time  $t$ .

- b. Determine the response of the mechanical system shown in Fig. 2 when subjected to the force  $f(t) = \begin{cases} 1, & 1 \leq t \leq 2 \\ 0, & \text{otherwise} \end{cases}$ , if  $M = 1 kg$ ,  $K = 2 Nm^{-1}$  and  $B = 3 Nm^{-1}s$

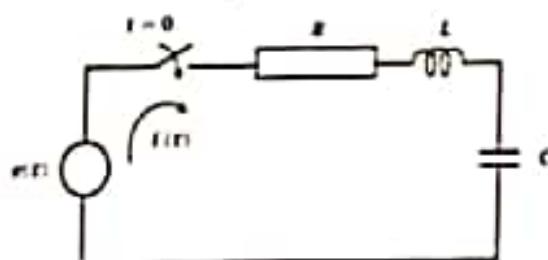


Fig. 1

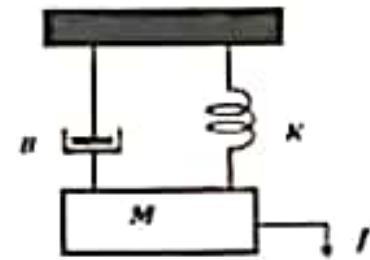


Fig. 2

**Question (3)**

{10 Marks}

- Find the general solution near  $x = 0$  of the variable coefficients linear differential equation (Bessel's equation):

$x^2 y'' + xy' + (x^2 - \frac{1}{4})y = 0$

With My Best wishes

# الورقة الأولى



التاريخ : 31 - 12 - 2018  
الزمن : 3 ساعت  
الفصل الدراسي : الأول

لجنة الامتحان الإلكترونية رقم : 101  
مدة : ٣٠ دقيقة (٣)  
شعبة المبرمجون والرياضيات الهمزة  
المرفق : الأولى

50 درجة

أجب عن جميع الأسئلة الآتية

السؤال الأول 20 درجة

(i) أوجد حل العام للخاص تمعنقة تناضية ثانية :

$$[x^2 y^2 - xy - y \sin x] dx + [x^3 y - x^2 + 2 \cos x] dy = 0, \quad y(0) = 1$$

إذا علم أن بها عامل مomial دائرة في  $y$  فقط

7 درجات

(ii) أوجد حل العام تمعنقة تناضية الآية ( معانة برتوس ) :

$$\frac{dy}{dx} + \frac{1}{x} y = (x^4 \sin x + x^2) y^4$$

(iii) استخدم طريقة بيكارد لحساب قيمة تقرير  $y$  ( التقرير الثالث ) عندما  $x = 0.02$ 

6 درجات

$$y' = x^2 + y, \quad y(0) = 1$$

السؤال الثاني 30 درجة

10 درجات

(i) أوجد الحل العام تمعنقة تناضية خطية الغرمتاجسة ثانية

( باستخدام طريقة تموير التناضي العكس في إيجاد الحل الخاص )

$$(D^3 + D^2 - D - 1)(D^2 - 2D + 5)y = e^{-x} + \sin(2x + 3)$$

10 درجات

(ii) أوجد الحل العام تمعنقة تناضية خطية الغرمتاجسة ثانية

( باستخدام طريقة تعميلات تغير معينة في إيجاد الحل الخاص )

$$y''' + 3y'' + 2y' = (x+2) + e^x + \cos 2x$$

10 درجات

(iii) أوجد الحل العام تمعنقة تناضية خطية الغرمتاجسة ثانية


( باستخدام طريقة تغير ابارمات في إيجاد الحل الخاص )

$$(x^3 D^3 - x^2 D^2 - 2x D + 6)y = x^5$$




أطيب التمنيات للجميع بالنجاح والتوفيق

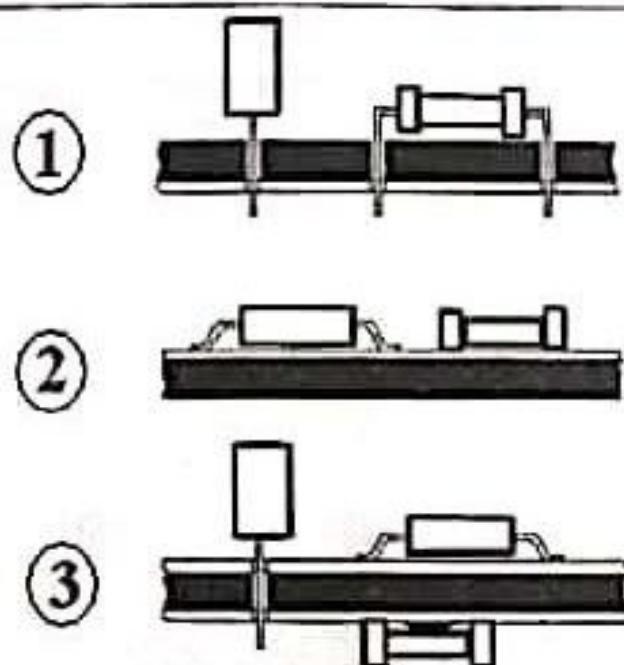١- اكتب طريقة اللحام المستخدمة في التربط الميكانيكي والتوصيل الكهربائي للعناصر في كل شكل من الاشكال التالية مع ذكر نوع الدائرة المطبوعة وأى عمليات اضافية ..... (٣ درجات)



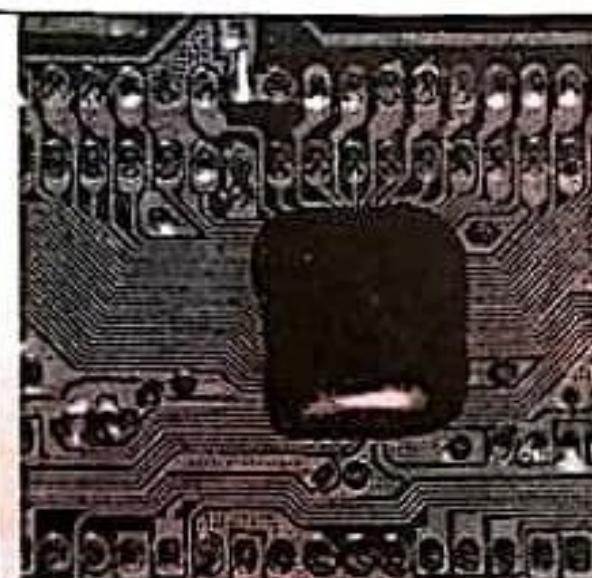٢- ما هي التكنولوجيا المستخدمة في هذا الشكل ؟ ارسم شكل تخطيطي يوضح مكونات ما تحت البقعة السوداء ..... (درجتان)





No of Questions: 4

No of Pages: 2

On June 2022/2024

*Answer the following questions:*

Total marks: 1600

---

*First question:*

1003

*Choose the correct answer.*



### *Second question:*

[20]

- (a) Write a function called *Count( )* that counts and returns the number of nodes in a linked list pointed by *head*.

اكتب ستة وصلات خرج وحدة الدائرة المطبوعة للربط مع ضفيرة الجهاز واتجاهاتها. (درجة واحدة)

رقم الطرف	الى	لون السك	من		لون السك
			رقم الطرف	رقم الوحدة	
		O			BK
		Y			BR
		GR			R

ارسم بالقلم الرصاص توزيع عناصر الواجهة الامامية لجهاز تنفيذية القدرة ..... (٣ درجات)

٣- باتسعة لمحول الكهربائي في الدائرة المذكورة ..... (درجة واحدة)

نوع المحول (متصفح أم بطيء)	تردد جهد التغذية
نوع مادة قلب المحول	أقصى تيار حمل
جيد النخل مقداره	جهد الخرج مقداره

٤- ارسم بالقلم الرصاص الدائرة التخطيطية لدائرة تغذية القراءة بعد رفع العناصر ذات التثبيت الميكانيكي المستقل.  
.....(درجتان)

## PART 2


- 1) For the circuit shown in Fig.1.

(10 marks)

$$V = 200 \sin \omega t$$

$$R_1 = R_2 = 10 \text{ k}\Omega,$$
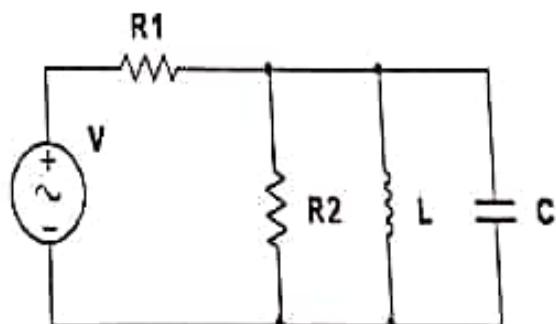
$$L = 0.1 \text{ mH and } C = 0.01 \mu\text{F}.$$



- Find the resonance frequency ( $\omega_0$ ).
- Calculate the R.M.S values of  $V_C$ ,  $I_L$  ( $\omega = \omega_0$ ).
- Find the active power delivered by the source at ( $\omega = \omega_0$ ).
- For ( $\omega = 2\omega_0$ ), determine whether the impedance circuit is inductive or capacitive.

Fig.1

- 2) For the circuit shown in Fig.2.

(10 marks)

$$V = V_m \sin \omega t$$

- Find an expression for the circuit impedance.
- Drive an expression for instantaneous power ( $P_i$ ) and average power ( $P_{avg}$ ) delivered by the source.
- Find the value of  $\omega$  that makes the impedance minimum.

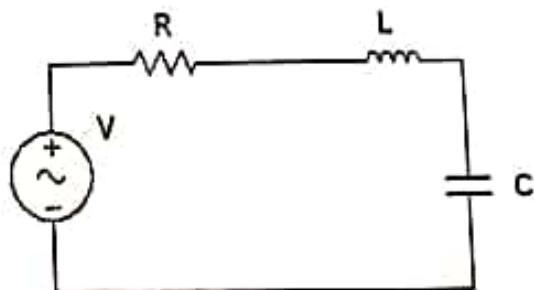


Fig.2

- 3) For the circuit shown in Fig.3.

(10 marks)

$$V = 50 \sin 2\pi ft, \quad F = 50 \text{ Hz}$$

$$R = 10 \Omega, \quad L = 10 \text{ mH}$$

- Find the value of  $C$  that makes the reactive power = 0.
- Find the R.M.S value of the current ( $I$ ).
- What is the phase shift between  $I$  and  $V$ ?

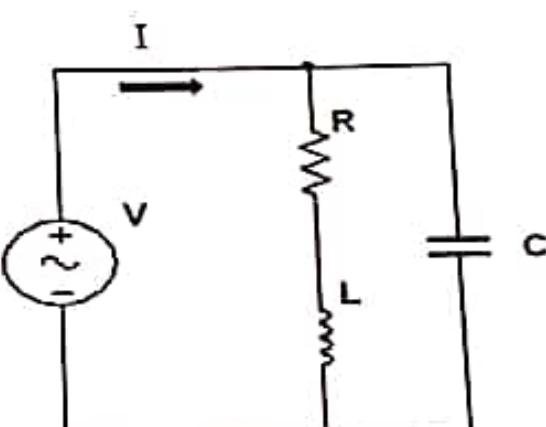


Fig.3

<b>University</b>	Menoufia
<b>Faculty</b>	Electronic Engineering
<b>Department</b>	General
<b>Academic Level</b>	1 <sup>st</sup> Year
<b>Academic Term</b>	1 <sup>st</sup> Term
<b>Course Name</b>	Electrical Engineering
<b>Course Code</b>	ACE 115
<b>Academic Year</b>	2017 - 2018



<b>Date</b>	14 /01/2018
<b>Time</b>	From 10 am to 1 pm
<b>No. of Pages</b>	2
<b>No. of Questions</b>	5
<b>Full Mark</b>	60
<b>Exam</b>	Final Exam
<b>Examiner</b>	Prof. Dr. Abdul-Azim S. Dr. Ramy Farid


**Answer all the following questions**

### **PART 1**

#### **Question 1**

**(15 marks)**

For the circuit in Figure 1, calculate total power delivered from the current source at maximum power transfer to  $R_L$ , and then sketch the characteristic curve of the total power delivered from the source by varying the load  $R_L$ .

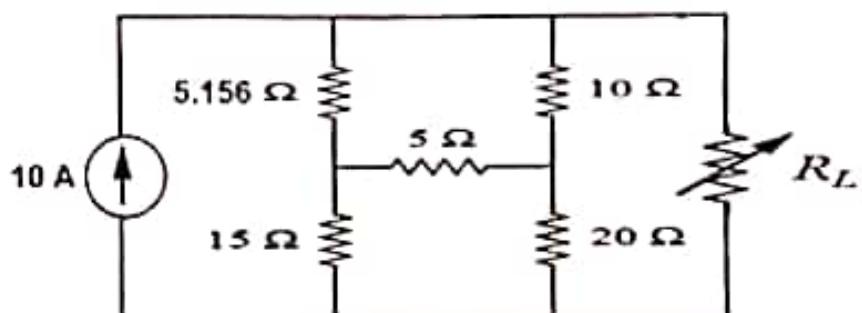

**Figure 1**


المادة: رسم العاكس والدوائر الإلكترونية  
عدد ملحوظات الأسئلة: (١)  
درجة الورقة الأولى: (٣٠ درجة)  
زمن الورقة الأولى: ساعة ونصف



الورقة الأولى (أ.د. / طه السيد طه)

كتبه انتهت الاختباراته بمتفوّف  
امتحان الفصل الدراسي الأول  
الورقة الأولى: (٢٠١٨/٢٠١٧)  
تاريخ الامتحان: ٢٠١٨ / ١ / ٣

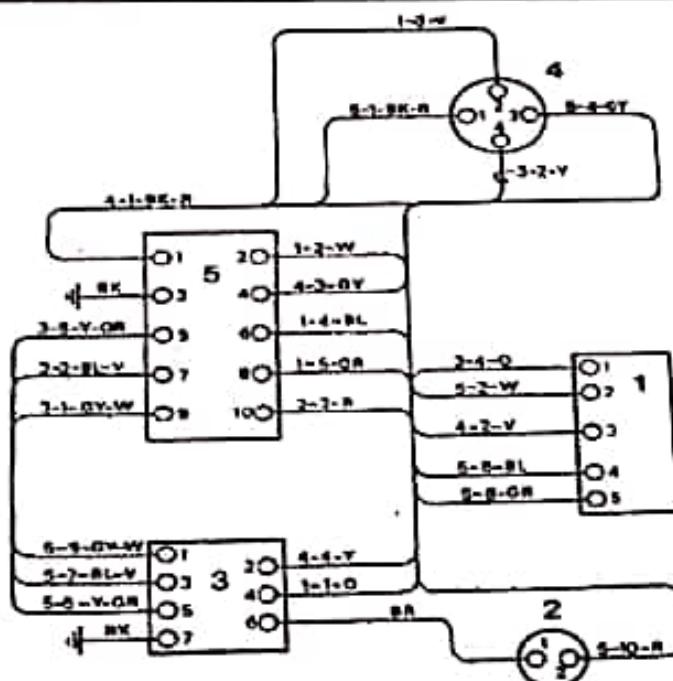
**ملحوظات هامة:** تقسم لوحة الرسم إلى أربعة أقسام وبخصوص قسم لكل شكل - تراعي قواعد رسم الدوائر الإلكترونية مع استخدام الأدوات الهندسية



أجب عن الأسئلة الآتية:

- ١- أرسم مخطط توصيل لشكل (١) بنظام التوصيل من نقطة إلى نقطة (Point-to-Point Diagram) (١٠ درجات)

الشكل (أ)

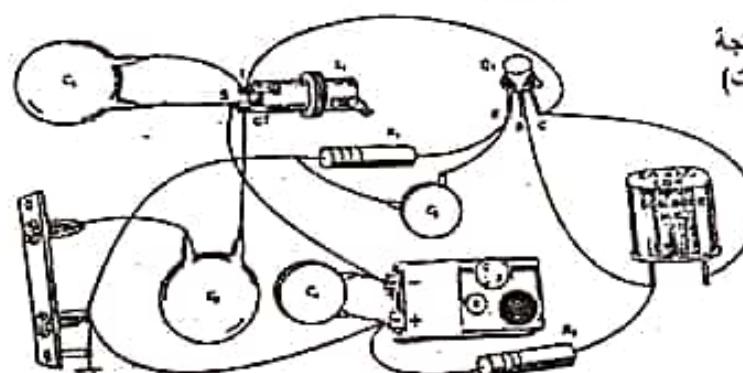


- ٢- أرسم الدائرة النظرية المستنيرة من الشكل (ب). (١٠ درجات)

الشكل (ب)

- ٣- الشكل (ج) يبين مجمع وأجزاء ملف خاتق والمطلوب رسم مسقط رأسى لقطاع كامل عند المنتصف بمقاييس رسم مناسب.  
(١٠ درجات)

أفق

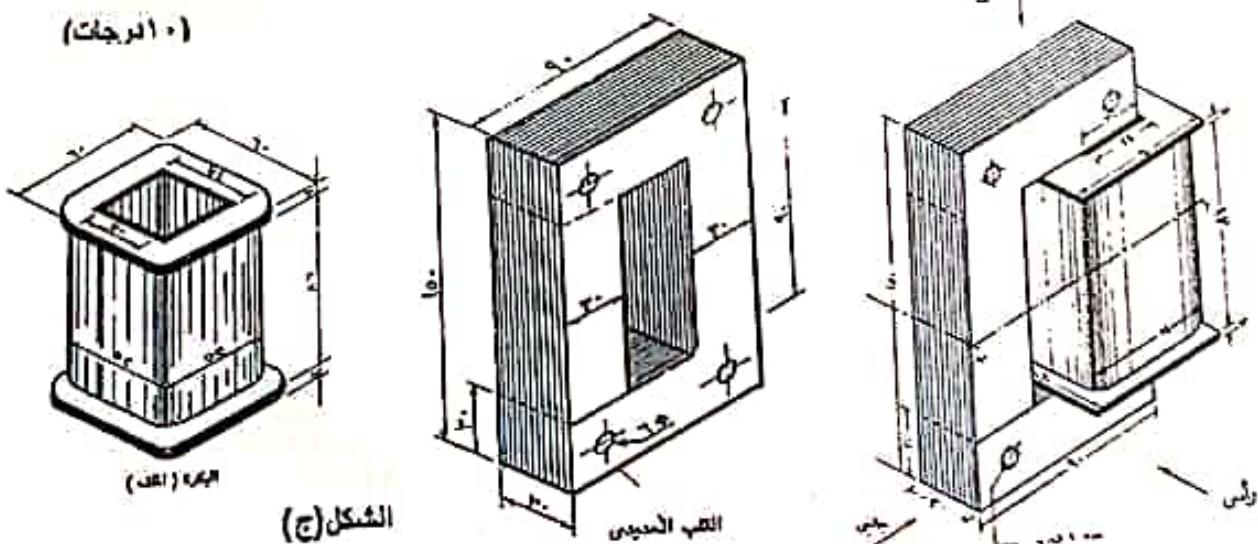

الشكل (ج)

---


**Answer all the following questions**

**PART 1**

**Question 1**

**(15 marks)**

For the circuit in Figure 1, calculate total power delivered from the current source at maximum power transfer to  $R_L$ , and then sketch the characteristic curve of the total power delivered from the source by varying the load  $R_L$

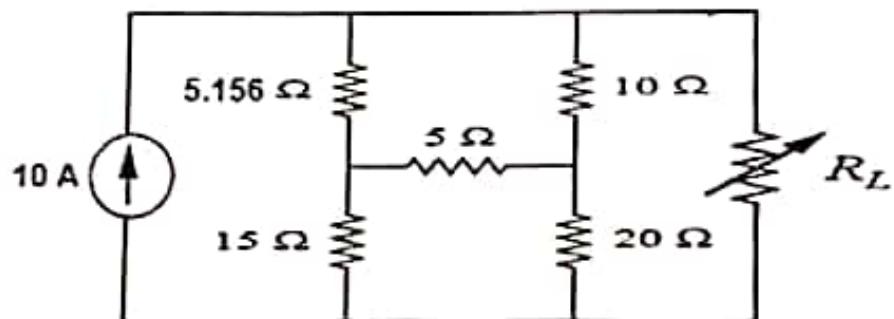

**Figure 1**

- 4-a) The  $K_{\alpha}$  and  $K_{\beta}$  X-rays of molybdenum have wavelengths 0.71 and  $0.63\text{\AA}$  respectively. Find the wavelength of  $L_{\alpha}$  X-ray of molybdenum. [5 Marks]
- 4-b) Calculate the corresponding thickness  $x$  required to reduce [10 Marks] the amount of transmitted X-ray intensity by half of Fe-17 mass % Cr alloy (density =  $7.76 \times 10^3 \text{ g/m}^3$  and mass absorption coefficients of Fe and Cr are 37.6 and  $29.9 \text{ cm}^2/\text{g}$  respectively for Mo- $K_{\alpha}$  radiation).
- 5-a) Convert the plane (101) into the four-index Miller-Bravais scheme for [5 Marks] hexagonal unit cells.
- 5-b) The unit cell for tin has tetragonal symmetry, with  $a$  and  $c$  lattice [10 Marks] parameters of 0.583 and 0.318 nm, respectively. If its density, atomic weight, and atomic radius are  $7.27 \text{ g/cm}^3$ , 118.71 g/mol, and 0.151 nm, respectively, compute the atomic packing factor.
- 6-a) Briefly explain the two possible origins of specific properties of [5 Marks] nanostructured materials.
- 6-b) The reflectivity of silicon at 633 nm is 35% and the absorption coefficient [10 Marks] is  $3.8 \times 10^5 \text{ m}^{-1}$ . Calculate the transmission and optical density of a sample with a thickness of  $10 \mu\text{m}$ .

Question	1(a)	1(b)	1(c)	2(a)	2(b)	2(c)	3(a)	3(b)	3(c)	4(a)	4(b)	5(a)	5(b)	6(a)	6(b)
Achieved ILOs	a1-5	b7-1	c1-2	a1-4	a1-3	b7-2	a1-3	a3-2	c1-2	a1-1	b2-2	a3-2	b2-1	a1-2	b2-3



Physical Constants:  $m_e = 9.1 \times 10^{-31} \text{ Kg}$      $e = 1.6 \times 10^{-19} \text{ C}$      $h = 6.6 \times 10^{-34} \text{ Js}$   
 $c = 3 \times 10^8 \text{ m/s}$      $k = 1.38 \times 10^{-23} \text{ J/K}$

*Answer the following questions:*

- 1-a) Discuss the physical meaning and the properties of the wave function ( $\psi$ ) according to quantum theory. [5Marks]
- 1-b) Consider an electron of mass (m) moving in x-direction in an infinite potential well of width (L), such that ( $V=0$ ) inside and ( $V=\infty$ ) outside the well. Find and draw the eigenfunctions, the eigenvalues and the probability of finding the electron for  $n = 1, 2, 3$ . [5Marks]
- 1-c) A photon with wavelength 0.5nm strikes an electron at rest and rebounds at angle of 120 to its original direction. Find the wavelength and speed of the photon after collision. [5Marks]

- 2-a) Define: 1-Degeneracy    2-Zeeman effect    3-Fermi energy level  
4-Pauli exclusion principle 5-Heisenberg uncertainty principle [5Marks]
- 2-b) Plot the potential energy of an electron in a linear periodic lattice and Kronig -Penny model. State the Bloch solution. [5Marks]
- 2-c) Calculate the probability of electron occupancy for state whose energy is:  
i) 0.2eV above Fermi energy level    ii) 0.2eV below Fermi energy level  
iii) equal to Fermi energy level  
Assume the temperature of 400K. [5Marks]

- 3-a) Explain the following:-  
i) Meissner effect    ii) Electron pairs formation in BCS theory [5Marks]
- 3-b) Compare between type I and type II superconductors. [5Marks]
- 3-c) Electrons with a maximum kinetic energy of 3eV are ejected from a metal surface by ultraviolet radiation of wavelength 1500A. Find:  
i) the work function of the metal  
ii) the threshold wavelength of the metal  
iii) the stopping potential [5Marks]

*Good luck*

*Dr.Ahmed Abo Arais*

**Question One (10 Marks)**

A1) Derive the complete hybrid equivalent circuit model for common Emitter transistor, and find an expression for the following parameters

- |                                 |                                  |
|---------------------------------|----------------------------------|
| 1. Total voltage gain           | 2. Total current gain            |
| 3. Input impedance of the stage | 4. Output impedance of the stage |

B1) The transistor shown in Fig. (1-1) has the following h-parameters values:  $h_{ie} = 2.75 \text{ K}\Omega$ ,  $h_{fe} = 180$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{oe} = 25 \mu\text{S}$ . Find (1)  $Z_{in}$ , (2)  $r_{in(\text{stage})}$  (3)  $A_v$ , (4)  $A_i$ , (5)  $A_{v(\text{total})}$ , and (6)  $Z_{o(\text{stage})}$ .

**Question Two (10 Marks)**

A2) Draw the DC load lines for the network of Fig. (1-2) on the characteristics of Fig. (1-3).

(B2) Determine the peak-to-peak value of  $I_c$  and  $V_{ce}$  from the graph if the input voltage  $V_i$  has a peak value of 10 mV. Determine the voltage gain  $A_v$ .

